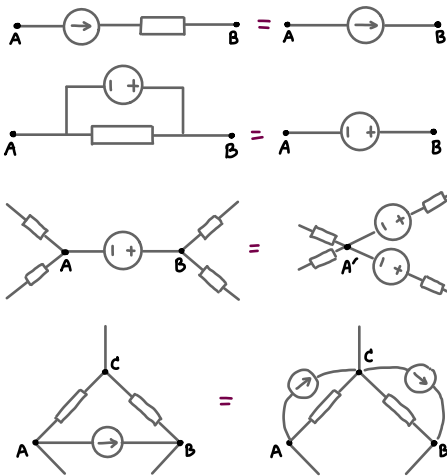



サーキット・ソーリー-II CIRCUIT THEORY II Midterm : Cheat sheet

① Source transformation

► Source relocation




► Thévenin-Norton transformation

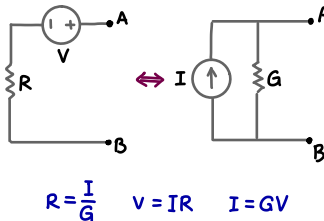


(Also works for dependent sources)

► Mutual inductance transformation

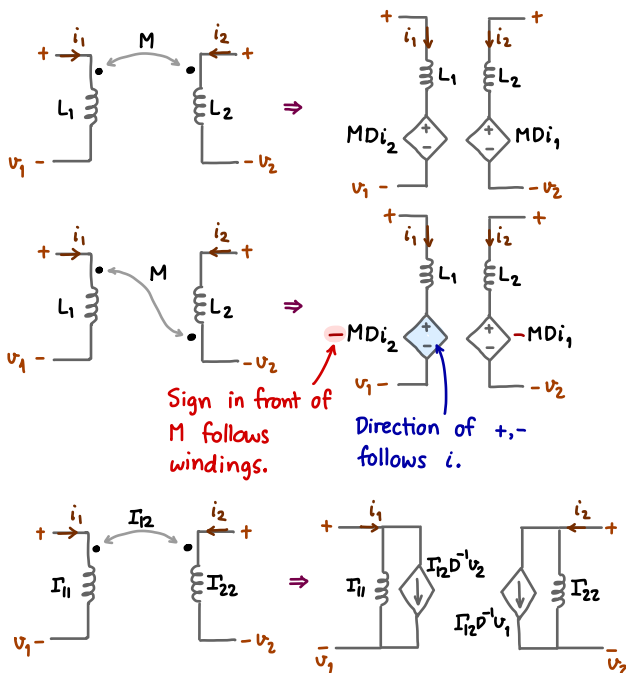

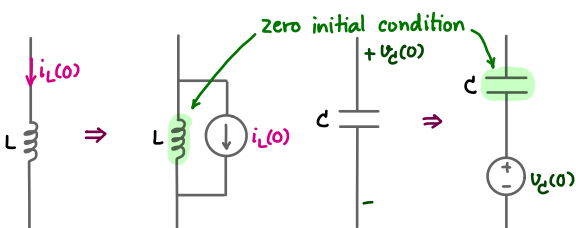► Initial condition to source transformation



② Nodal analysis

• Systematic method

- 1) Perform source transformation.
- 2) Draw digraph, choose one reference node and write down reduced incidence matrix A.

$$A = [a_{ij}]$$

$$a_{ij} = \begin{cases} 0 & \text{if node } i \text{ is not connected to branch } j \\ 1 & \text{if node } i \text{ is the tail of branch } j \\ -1 & \text{if node } i \text{ is the head of branch } j \end{cases}$$

- 3) Find branch equations, then write them in a matrix form.

$$\begin{cases} \text{One branch: } i_k = Y_{bk} v_k + i_{sk} - Y_{bk} v_s \\ \text{Every branches: } i = Y_b v + i_s - Y_b v_s \end{cases}$$

(Matrix form)

- 4) Find $Y_n \triangleq AY_b A^T$ and $I_{ss} \triangleq AY_b v_s - A i_s$, the node equations are $Y_n e = I_{ss}$.

Node voltages

- 5) Find the initial condition of $e \cdot e(0)$.

• Inspection method

- 1) Try to transform everything to current sources.

- 2) Find Y'_n, I'_{ss} .

Diagonal entries = sum of admittances around node i

Y'_n is symmetric matrix $\rightarrow Y'_n = \begin{bmatrix} y_{11} & y_{12} & \dots & y_{1n} \\ y_{21} & y_{22} & \dots & y_{2n} \\ \vdots & \vdots & \ddots & \vdots \\ y_{n1} & y_{n2} & \dots & y_{nn} \end{bmatrix}$

Entries not in main diagonal = sum of negative of admittance between i, j

I'_{ss} is column vector $\rightarrow I'_{ss} = \begin{bmatrix} i'_{ss1} \\ i'_{ss2} \\ i'_{ss3} \\ \vdots \\ i'_{ssn} \end{bmatrix}$

Combinations of current sources around node i

add when \rightarrow

subtract when \leftarrow

- 3) Express $I'_{ss} = I_{ss} + Y_c e$

Admittance matrix from current sources.

- 4) Let $Y_n = Y'_n - Y_c$. the node equations are $Y_n e = I_{ss}$.

- 5) Find the initial condition of $e \cdot e(0)$.


Note : Initial conditions of e are only dependent to $R, L, C, v_s, i_s, i_L(0)$ and $v_C(0)$.

Sources

③ Mesh analysis

• Systematic method

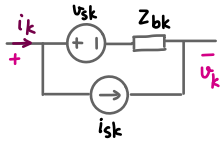- 1) Perform source transformation.
- 2) Draw digraph, draw mesh currents and write down mesh matrix M .
- 3) Find branch equations, then write them in a matrix form.



One branch: $v_k = Z_{bk} i_k + v_{sk} - Z_{bk} i_{sk}$
 Every branches: $v = Z_b i + v_s - Z_b i_s$
 (Matrix form)

$$M = [m_{ij}]$$

$$m_{ij} = \begin{cases} 0, & \text{if } i \text{ and } j \text{ are not in the same mesh} \\ 1, & \text{if } i \text{ and } j \text{ are in the same mesh and the current flows in the same direction} \\ -1, & \text{if } i \text{ and } j \text{ are in the same mesh and the current flows in opposite directions} \end{cases}$$

- 4) Find $Z_m = M Z_b M^T$ and $E_s = M Z_b i_s - M v_s$, the mesh equations are $Z_m j = E_s$.

Mesh current

- 5) Find the initial condition of j : $j(0)$

• Inspection method

- 1) Try to transform everything to voltage sources.
- 2) Find Z'_m, E'_s .

Z'_m is symmetric matrix $\rightarrow Z'_m =$

$$\begin{bmatrix} z_{11} & z_{12} & \dots & z_{1n} \\ z_{21} & z_{22} & \dots & z_{2n} \\ \vdots & \vdots & \ddots & \vdots \\ z_{n1} & z_{n2} & \dots & z_{nn} \end{bmatrix}$$

Diagonal entries = sum of impedance around mesh i
 Entries not in main diagonal = sum of negative of impedance between mesh i, j

E'_s is column vector $\rightarrow E'_s =$

$$\begin{bmatrix} e'_{s1} \\ e'_{s2} \\ e'_{s3} \\ \vdots \\ e'_{sn} \end{bmatrix}$$

Combinations of voltage sources around mesh i
 add when \rightarrow (positive voltage source)
 subtract when \rightarrow (negative voltage source)

- 3) Express $E'_s = E_s + Z_v j$.

- 4) Let $Z_m = Z'_m - Z_v$. the node equations are $Z_m j = E_s$.

- 5) Find the initial condition of j : $j(0)$.

Node/Mesh Response

Node Equation

$$Y_n(D) e(t) = I_{ss}(t) \quad \text{initial condition}$$

$$\mathcal{L}; Y_n(s) E(s) = I_{ss}(s) + I_i$$

$$\text{Complete Response: } E(s) = \underbrace{Y_n(s)^{-1} I_{ss}(s)}_{\text{ZSR}} + \underbrace{Y_n(s)^{-1} I_i}_{\text{ZIR}}$$

Mesh Equation

$$Z_m(D) j(t) = E_{ss}(t) \quad \text{initial condition}$$

$$Z_m(s) J(s) = E_{ss}(s) + E_i$$

$$J(s) = \underbrace{Z_m(s)^{-1} E_{ss}(s)}_{\text{ZSR}} + \underbrace{Z_m(s)^{-1} E_i}_{\text{ZIR}}$$

State Response

$$\text{State Equation } \dot{x} = Ax + Bu$$

$$\mathcal{L}; sX(s) - x(0) = AX(s) + BU(s) \quad \text{isun Resolvent Matrix}$$

$$X(s) = \underbrace{(sI - A)^{-1} x(0)}_{\text{ZIR}} + \underbrace{(sI - A)^{-1} BU(s)}_{\text{ZSR}}$$

④ State equations

$$\left. \begin{aligned} x &= \text{state vector} \\ u &= \text{input vector} \\ y &= \text{output vector} \end{aligned} \right\}$$

State equations:


$$\dot{x} = Ax + Bu$$

Output equations:

$$y = Cx + Du$$

In LTI circuit, state variables often be the inductor currents and capacitor voltages.

How to: write state, output equations.

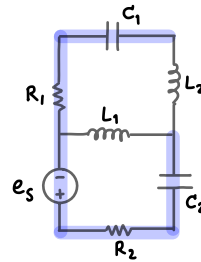

- 1) Pick a tree that contains all capacitors and no inductor.

Ex: Tree $\{C_1, R_1, e_s, R_2, C_2\}$

- 2) If the state variables are not given, use capacitor voltages and inductor currents as the state variables.

These equations must be expressed in terms of chosen variables in step (2) and input variables.

- 3) Write a cut-set equation or KCL for each capacitor.
- 4) Write a loop equation or KVL for each inductor.

- 5) Rearrange the equations in step (3), (4) to obtain state equations $\dot{x} = Ax + Bu$.

- 6) Write down the outputs in terms of state variables and inputs and obtain output equations $y = Cx + Du$.

ตารางผลการแปลงลาปลาซ

$f(t)$	$F(s)$
$\delta(t)$	1
1	$\frac{1}{s}$
t	$\frac{1}{s^2}$
t^2	$\frac{2}{s^3}$
t^n	$\frac{n!}{s^{n+1}}$
e^{-at}	$\frac{1}{s+a}$
$\sin \omega t$	$\frac{\omega}{s^2 + \omega^2}$
$\cos \omega t$	$\frac{s}{s^2 + \omega^2}$
$e^{-at} \sin \omega t$	$\frac{\omega}{(s+a)^2 + \omega^2}$
$e^{-at} \cos \omega t$	$\frac{s+a}{(s+a)^2 + \omega^2}$
$e^{-at} \cosh(\omega t)$	$\frac{s+a}{(s+a)^2 - \omega^2}$
$e^{-at} \sinh(\omega t)$	$\frac{\omega}{(s+a)^2 - \omega^2}$